

Circuit Analysis


Section 04

Ohm's Law



- A current through a resistor is proportional to the voltage across its terminals
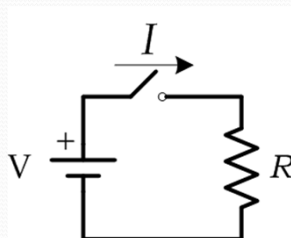
$$V = I \cdot R \quad \text{or} \quad I = \frac{V}{R}$$




$$R \rightarrow \infty \quad I = 0$$

$$R \rightarrow 0 \quad I = \infty$$


Short a 1.5 battery, what will happen?

Internal Resistance

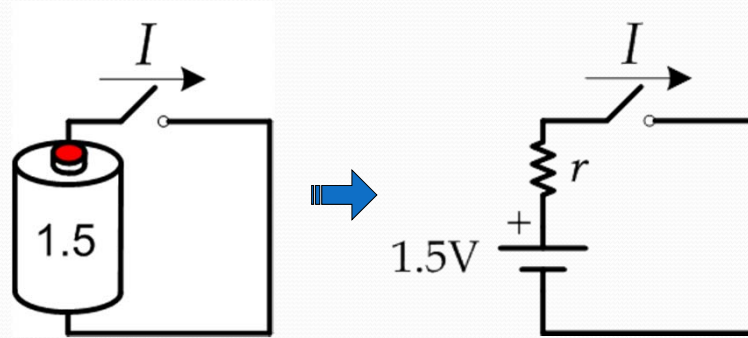- If you short a 1.5V battery, how much current will pass?




Overloading

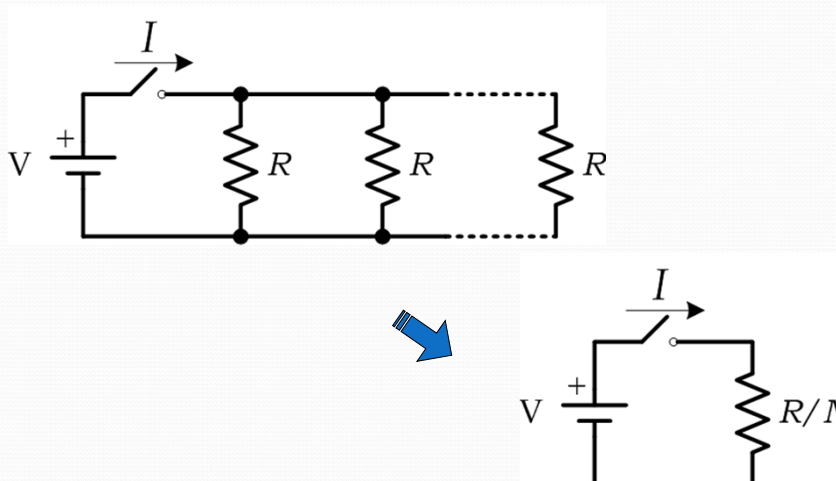

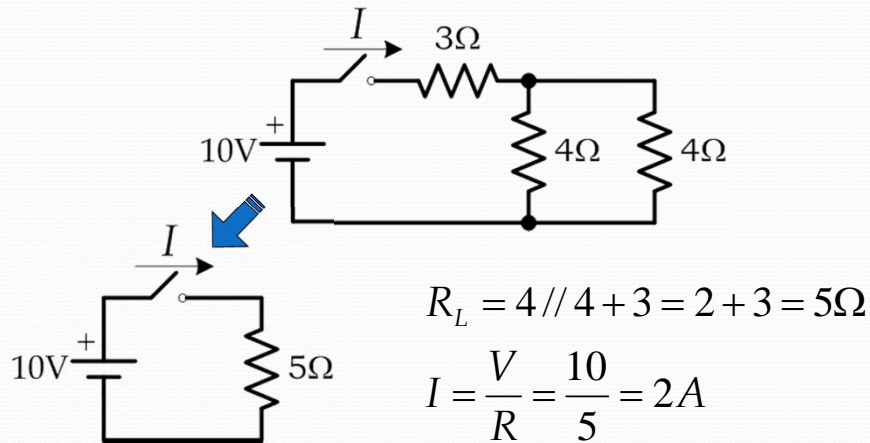Question

- What is the total current drawn from the source?




Electrical & Computer Engineering

King Abdulaziz University

Slide 87

Voltage Divider

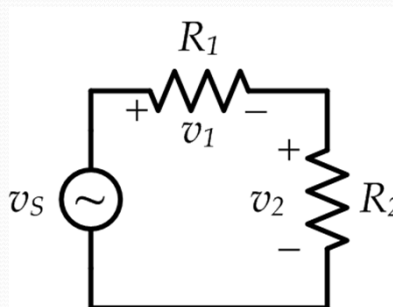

$$v_1 = v_s \frac{R_1}{R_1 + R_2}$$


$$v_2 = v_s \frac{R_2}{R_1 + R_2}$$

Electrical & Computer Engineering

King Abdulaziz University

Slide 88


Current Divider

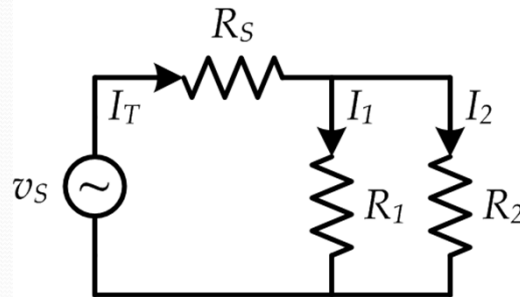

$$I_1 = I_T \frac{R_2}{R_1 + R_2}$$


$$I_2 = I_T \frac{R_1}{R_1 + R_2}$$

Multiple Loads

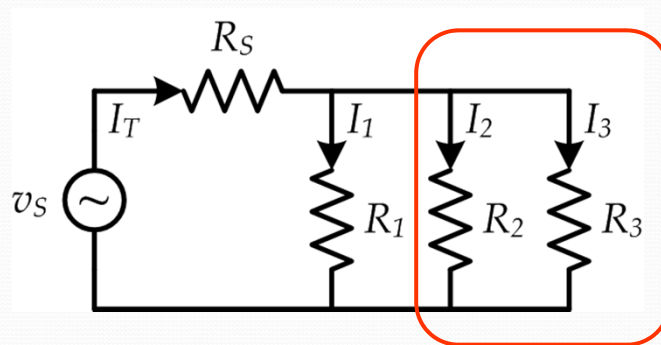

Combine Parallel Loads

Multiple Loads

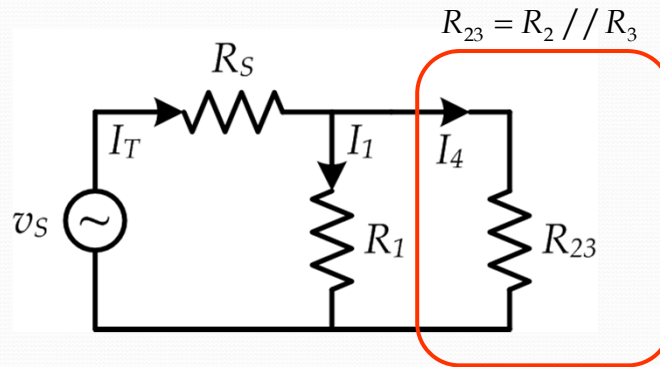

$$I_1 = I_T \frac{R_{23}}{R_1 + R_{23}}$$


$$I_4 = I_T \frac{R_1}{R_1 + R_{23}}$$

Electrical & Computer Engineering

King Abdulaziz University

Slide 91

Multiple Loads

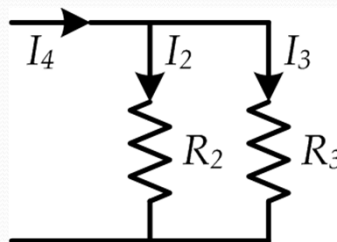

$$I_2 = I_4 \frac{R_3}{R_2 + R_3}$$


$$I_3 = I_4 \frac{R_2}{R_2 + R_3}$$

Electrical & Computer Engineering

King Abdulaziz University

Slide 92

Current Divider

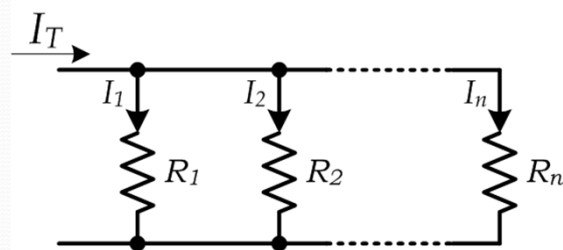

$$R_p = R_1 // R_2 // \dots // R_n$$

$$I_k = I_T \frac{R_p}{R_k}$$


Electrical & Computer Engineering

King Abdulaziz University

Slide 93

Process Check

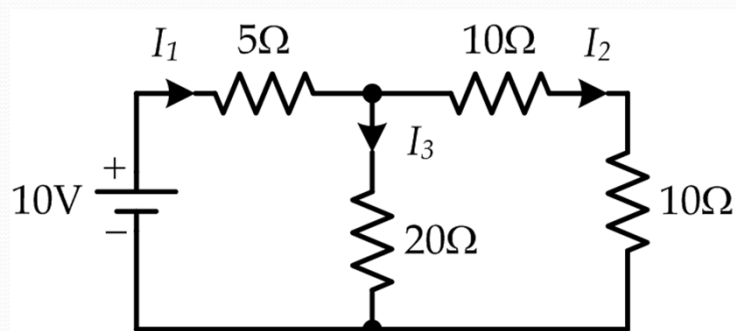- Calculate all currents in the circuit..
 - What is your plan?!




Electrical & Computer Engineering

King Abdulaziz University

Slide 94

Multiple Sources

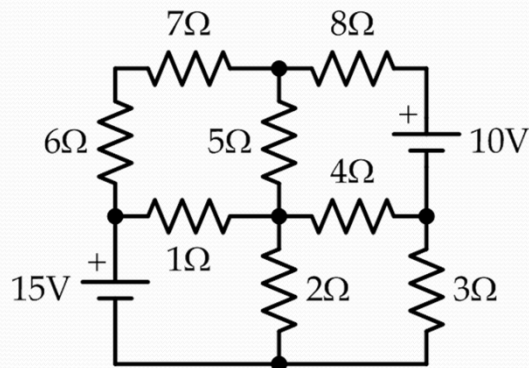- What if more than one source in the circuit?
 - How to solve for all currents?




Electrical & Computer Engineering

King Abdulaziz University

Slide 95

Nodes and Loops

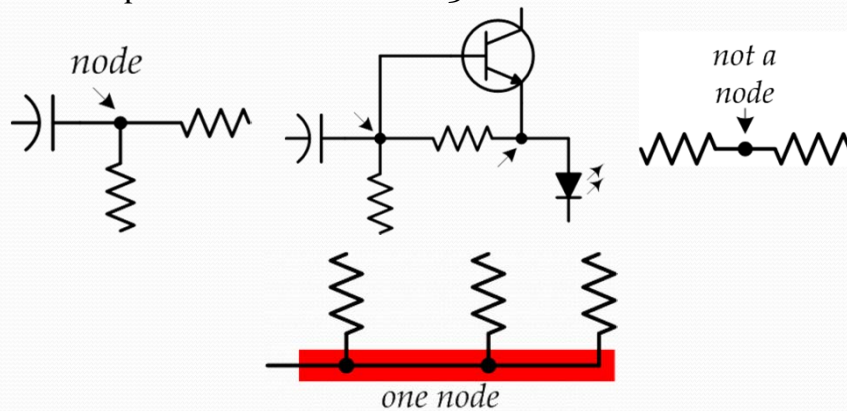- A Node
 - a point in a circuit where 3 or more elements meet




Electrical & Computer Engineering

King Abdulaziz University

Slide 96

Nodes and Loops

- How many nodes in the circuits?

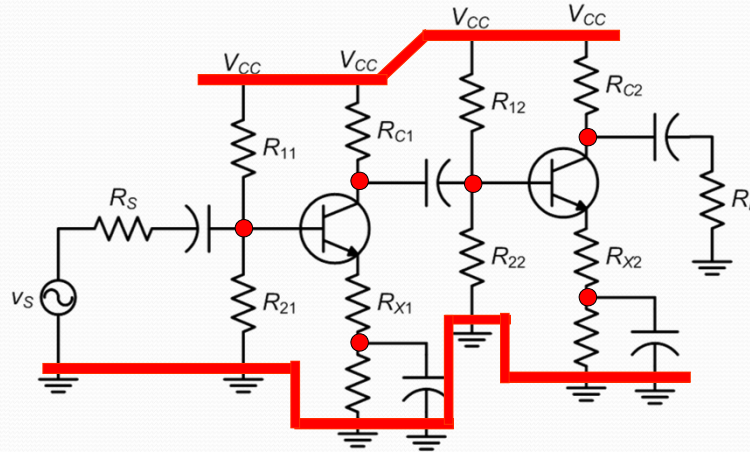


Electrical & Computer Engineering

King Abdulaziz University

Slide 97

Nodes and Loops

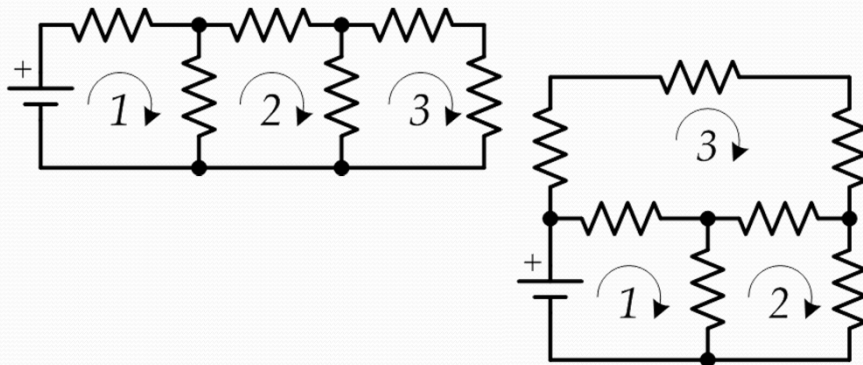- A Loop:
 - a closed ring in a planer circuit




Electrical & Computer Engineering

King Abdulaziz University

Slide 98

Planer Circuit

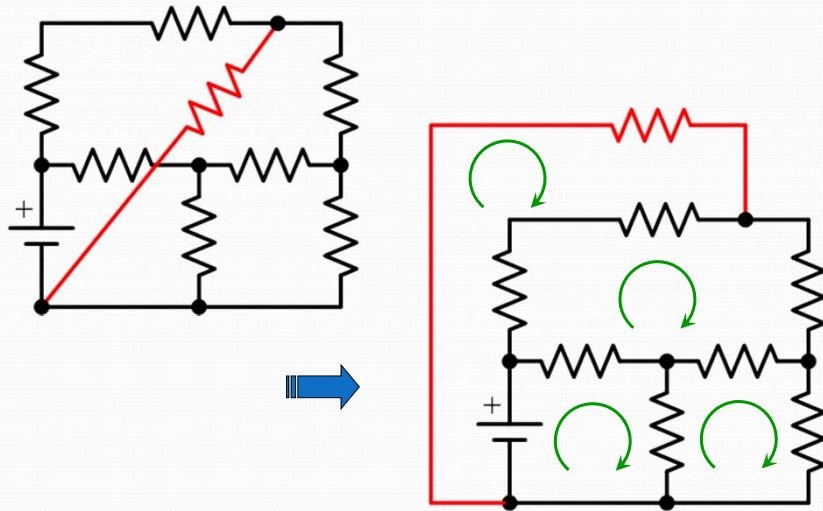


Electrical & Computer Engineering

King Abdulaziz University


Slide 99

Voltage Drop

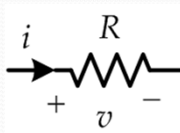- A current passing through a load generates a voltage drop



$$v = i \cdot R$$

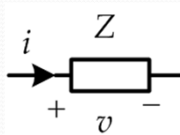

$$v = i \cdot Z$$

Electrical & Computer Engineering

King Abdulaziz University

Slide 100

KVL and KCL




- *(nodes, loops, planner circuit, voltage drop) then what?*
- To solve for all currents and volts in a circuit:
 - KVL: Kirchhoff's Voltage Law
 - the algebraic sum of voltages in a loop is zero
 - KCL: Kirchhoff's Current Law
 - the algebraic sum of currents into a node is zero

Circuit Analysis



1. count nodes minus one (possible ground)
2. mark a current for each branch
 - name and direction
3. write KCL equations for each node
4. count the loops
5. write the KVL equations for each loop
6. solve for all unknowns

Example

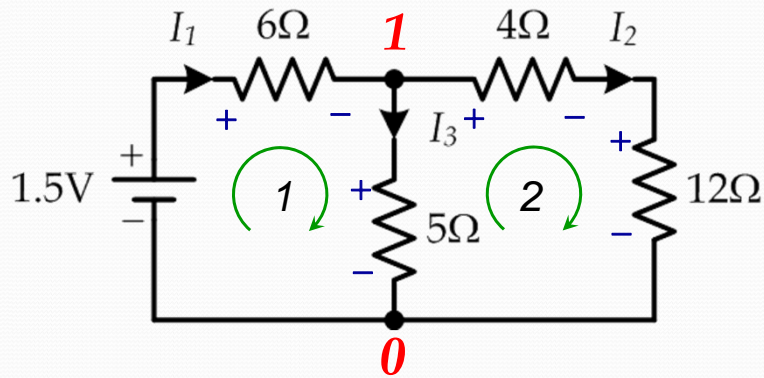


Electrical & Computer Engineering

King Abdulaziz University

Slide 103

Example

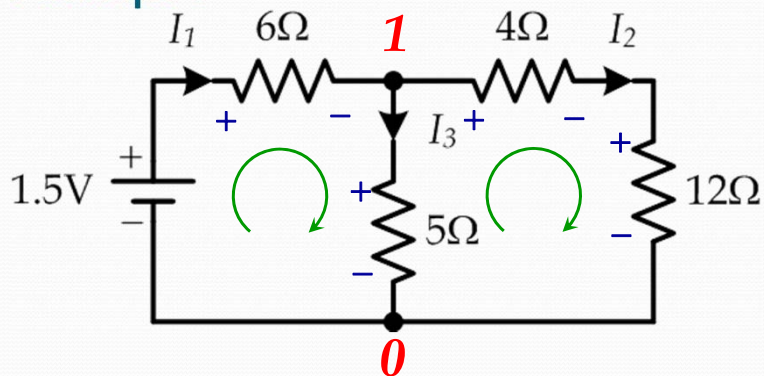

$$KCL: I_1 = I_2 + I_3$$

$$KVL: \begin{aligned} -1.5 + 6I_1 + 5I_3 &= 0 \\ -5I_3 + 4I_2 + 12I_2 &= 0 \end{aligned}$$




$$\begin{aligned} I_1 &= 152.9 \text{ mA} \\ \Rightarrow I_2 &= 36.4 \text{ mA} \\ I_3 &= 116.5 \text{ mA} \end{aligned}$$

Electrical & Computer Engineering

King Abdulaziz University

Slide 104

Example

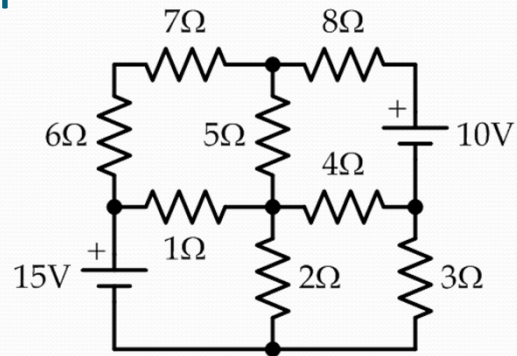

8 branches \rightarrow 8 currents $I_1..I_8 \rightarrow$ 8 equations

4 nodes \rightarrow 4 eqs

4 loops \rightarrow 4 eqs