
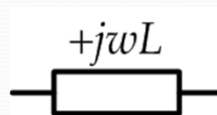
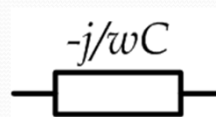


Complex Impedance

Section 05

Impedance

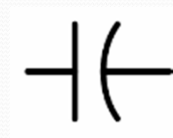- treat all passive components as resistors
 - but with *complex* resistances



Impedance



- What is the impedance of a $10\mu\text{F}$ capacitor when operated at 60Hz ?

$$Z_C = -\frac{j}{\omega C} = -\frac{j}{2\pi \times 60 \times 10 \times 10^{-6}} = -j265.25\Omega$$

- What is the impedance of a 2mH inductor when operated at 60Hz ?

$$Z_L = j\omega L = j2\pi \times 60 \times 2 \times 10^{-3} = +j0.754\Omega$$

Laplace Domain




- When
 - Mixing AC and DC sources
 - Multiple different frequencies
- use Laplace instead of Fourier
 - $j\omega \rightarrow s$
 - *Initial conditions*

Complex AC Source

- AC Volt or Current has:

- Amplitude
- Frequency
- Phase

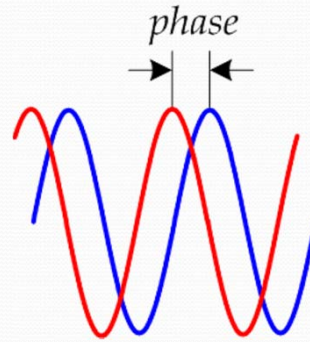- Phase can be expressed in Complex Number



$$A \cos(2\pi f \cdot t + \varphi) \rightarrow A \angle \varphi$$


Complex AC Source

$$A \cos(2\pi f \cdot t + \varphi)$$

$$A \angle \varphi \rightarrow A \cdot (\cos \varphi + j \sin \varphi)$$

$$110 \angle 30^\circ \rightarrow 110 \cdot (\cos 30^\circ + j \sin 30^\circ) \\ = 95.26 + j55$$

Example

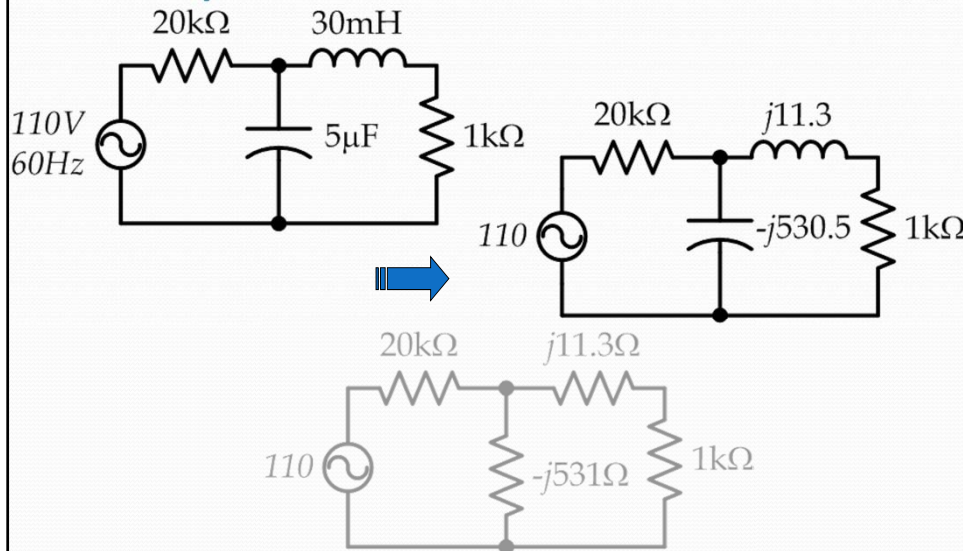

Electrical & Computer Engineering

King Abdulaziz University

Slide 113

Solution

$$KCL: I_1 = I_2 + I_3$$

$$KVL: \begin{aligned} -110 + 20,000 \times I_1 - j531 \times I_3 &= 0 \\ +j531 \times I_3 + j11.3 \times I_2 + 1000 \times I_2 &= 0 \end{aligned}$$


$$\begin{aligned} I_1 &= 5.44 \angle +1.2^\circ \text{ mA} \\ \Rightarrow I_2 &= 2.56 \angle -61.4^\circ \text{ mA} \\ I_3 &= 4.83 \angle +29.3^\circ \text{ mA} \end{aligned}$$

Electrical & Computer Engineering

King Abdulaziz University

Slide 114

Simulation Solution

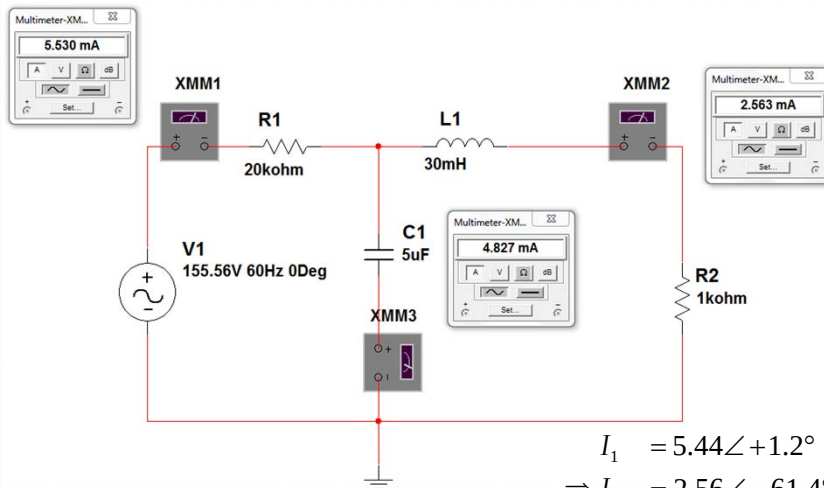

$$\begin{aligned} I_1 &= 5.44 \angle +1.2^\circ \text{ mA} \\ \Rightarrow I_2 &= 2.56 \angle -61.4^\circ \text{ mA} \\ I_3 &= 4.83 \angle +29.3^\circ \text{ mA} \end{aligned}$$



Electrical & Computer Engineering

King Abdulaziz University

Slide 115

Current Source

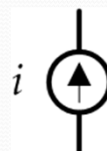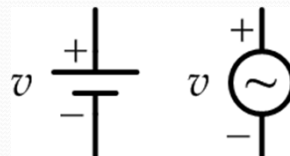- Voltage Source
 - Generates **constant** volt regardless of the load
- Current Source
 - Generates **constant** current regardless of the load




Electrical & Computer Engineering

King Abdulaziz University

Slide 116

KVL & KCL

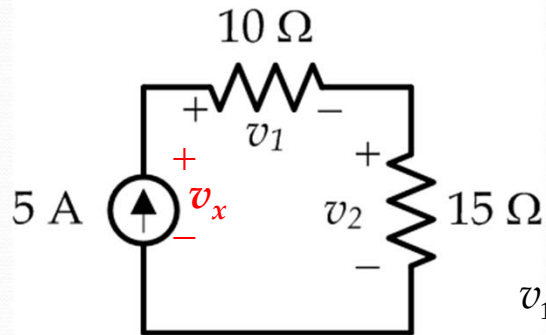


$$v_1 = 5 \times 10 = 50V$$

$$v_2 = 5 \times 15 = 75V$$

$$v_x = v_1 + v_2$$

Example

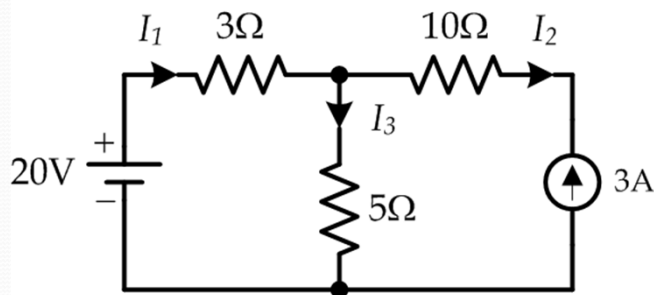

$$KCL: I_1 = I_2 + I_3 \quad I_1 = 0.625 \quad A$$

$$KVL: -20 + 3I_1 + 5I_3 = 0 \quad \Rightarrow \quad I_2 = -3 \quad A$$

$$-5I_3 + 10I_2 + v_i = 0 \quad I_3 = 3.625 \quad A$$

$$IS: I_2 = -3A \quad v_i = 48.125 \quad V$$

Power




- Power = rate of energy transfer
 - measured in Watts (W)

$$P = I \cdot V$$

$$P = I \cdot V = I^2 \cdot R$$

$$P = I \cdot V = \frac{V^2}{R}$$

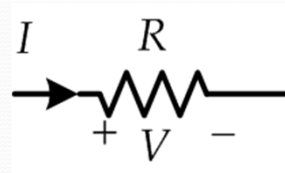

Instantaneous Power



- instantaneous power, $p(t)$

$$p(t) = v(t) \times i(t)$$

- for general AC signals:

$$v(t) = V_p \cos(2\pi f \cdot t + \theta_v)$$

$$i(t) = I_p \cos(2\pi f \cdot t + \theta_i)$$

Average Power

$$\begin{aligned} P &= \frac{1}{T} \int_0^T v(t) \times i(t) dt \\ &= \frac{1}{T} \int_0^T V_p \cdot I_p \times [\cos(2\pi f \cdot t + \theta_V) \cdot \cos(2\pi f \cdot t + \theta_I)] dt \\ &= \frac{1}{T} \int_0^T \frac{V_p \cdot I_p}{2} \times [\cos(\theta_V - \theta_I) + \cos(4\pi f \cdot t + \theta_V + \theta_I)] dt \\ &= \frac{V_p \cdot I_p}{2T} \cos(\theta_V - \theta_I) \times \int_0^T [1 + \cos(4\pi f \cdot t + \theta_V + \theta_I)] dt \\ &= \frac{V_p \cdot I_p}{2T} \cos(\theta_V - \theta_I) \times T \\ &= V_{RMS} \cdot I_{RMS} \times \cos(\theta_V - \theta_I) \end{aligned}$$

Real Power

- thus, the real power is:

$$P = V_{RMS} \cdot I_{RMS} \times PF$$

- where, the power factor is:

$$PF = \cos(\theta_V - \theta_I)$$

Reactive Power



- Define 'S' as the total volt-ampere

$$S = I^* \cdot V = P + jQ$$

where (V) and (I) in complex form and RMS values


- Example:

$$\begin{array}{rcl} I & = & 3 + j5 \\ V & = & 9 - j7 \end{array} \Rightarrow \begin{array}{rcl} S & = & (3 - j5) \cdot (9 - j7) = -8 - j66 \\ P & = & -8W \\ Q & = & -66VA \end{array}$$


Process Check



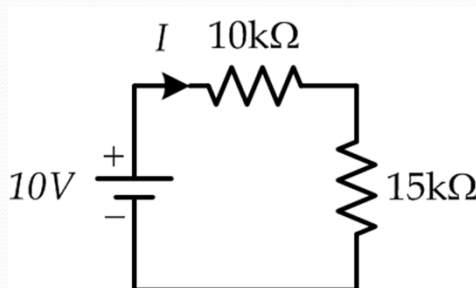- Solve the circuit shown and find the power consumption of each component



Solution (1)

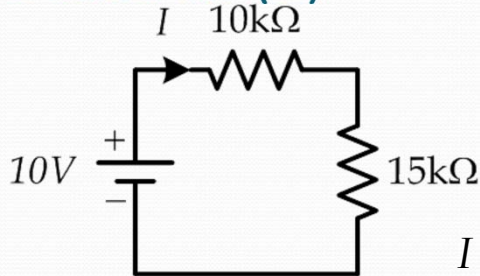


$$I = \frac{10}{10k + 15k} = 400\mu A$$

$$P_1 = I^2 \cdot R_1 = (400 \times 10^{-6})^2 \cdot 10 \times 10^3 = 1.6mW$$

$$P_2 = I^2 \cdot R_2 = (400 \times 10^{-6})^2 \cdot 15 \times 10^3 = 2.4mW$$

Solution (2)

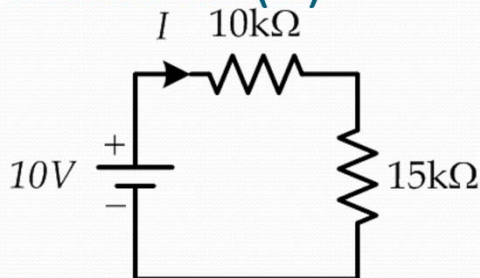


$$V_1 = 10 \frac{10k}{10k + 15k} = 4V$$

$$V_2 = 10 \frac{15k}{10k + 15k} = 6V$$

$$P_1 = \frac{V_1^2}{R_1} = \frac{4^2}{10 \times 10^3} = 1.6mW$$

$$P_2 = \frac{V_2^2}{R_2} = \frac{6^2}{15 \times 10^3} = 2.4mW$$


Total Power = 0

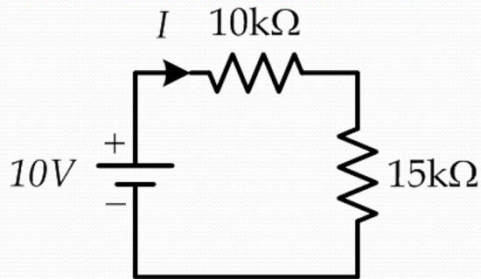

$$P_s = I \cdot V = -400 \times 10^{-6} \cdot 10 = -4mW$$

$$P_1 + P_2 = 4mW \quad \text{Total Power = Zero}$$

Example

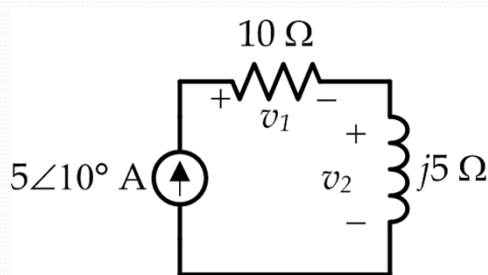


$$V_1 = 50 \angle 10^\circ$$

$$V_2 = 25 \angle 100^\circ$$

$$V_s = V_1 + V_2 = 56 \angle 36.6^\circ$$

$$S_s = -I_s^* \cdot V_s = -280 \angle 26.6^\circ = -250 - j125$$

Example

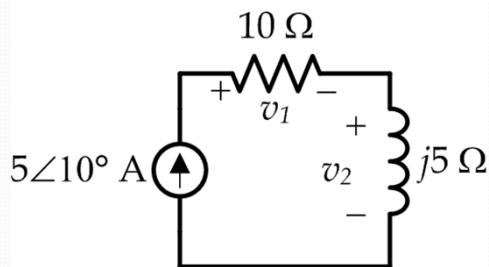

$$S_R = I_S^* \cdot V_1 = (5\angle -10^\circ) \times (50\angle 10^\circ) = 250 + j0$$

$$S_L = I_S^* \cdot V_2 = (5\angle -10^\circ) \times (25\angle 100^\circ) = 0 + j125$$

Total Power = Zero