
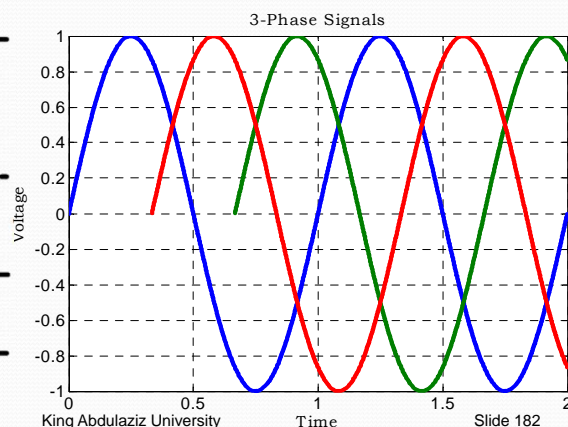


3-Phase Systems

Section 09

3-Phase Generators

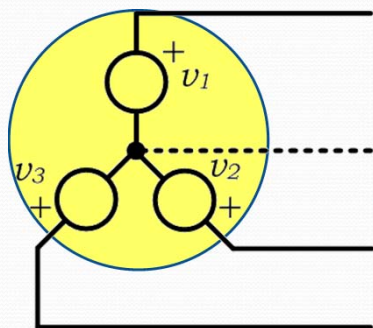- Method for transmitting alternating power
- Three conductors carrying three alternating currents with $360/3=120^\circ$ shift between them



Electrical & Computer Engineering


King Abdulaziz University

Time

Slide 182

Why 3 ϕ System?

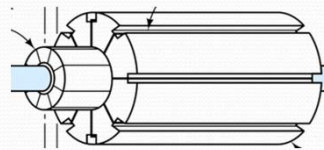- Multi-Phase Generation
 - constant power generation all the time
 - cost effective
- Usage
 - 1 ϕ of each phase at homes
 - 3 ϕ loads at industry




Electrical & Computer Engineering

King Abdulaziz University


Slide 183

Vector Representation

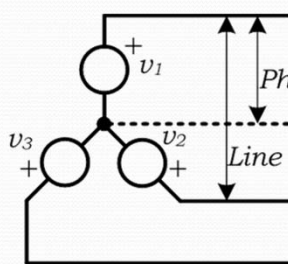

Phase Voltage

Line Voltage

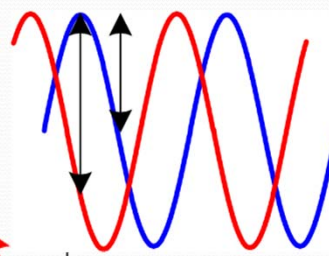

$1 \angle 120^\circ$

$1 \angle 0^\circ$

$1 \angle 240^\circ$

V_{line}

Electrical & Computer Engineering

King Abdulaziz University

Slide 184

Line Voltage



$$\begin{aligned}v_{12} &= v_1 - v_2 \\&= 1\angle 0^\circ - 1\angle 120^\circ \\&= 1 - (\cos 120 + j \sin 120) \\&= \frac{3}{2} - j \frac{\sqrt{3}}{2}\end{aligned}$$

$$v_{12} = \sqrt{3}\angle -30^\circ$$

$$v_{23} = \sqrt{3}\angle +90^\circ$$


$$v_{31} = \sqrt{3}\angle -150^\circ$$

Examples



- If a phase voltage is 120V~
 - Line Voltage = $120 \cdot \sqrt{3} = 208V \sim$
- If a line voltage is 220V~
 - Phase Voltage = $220 / \sqrt{3} = 127V \sim$

Load Distribution

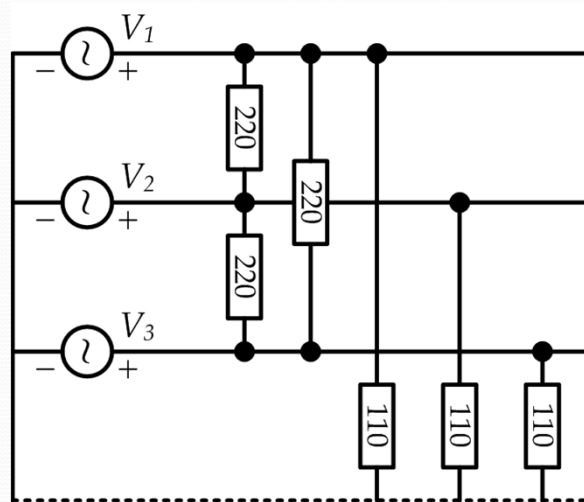


Electrical & Computer Engineering

King Abdulaziz University

Slide 187

Star-Start Connection

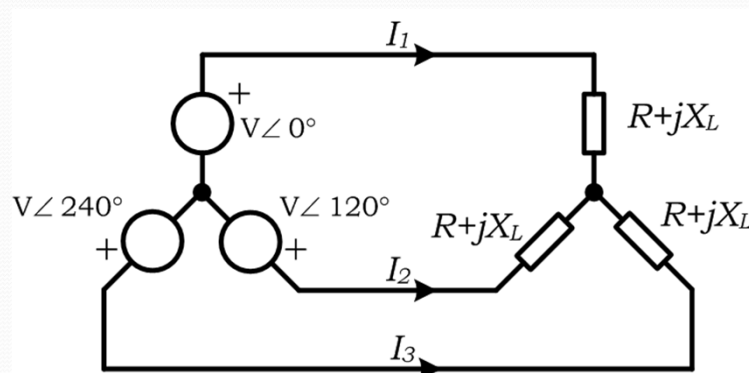


Electrical & Computer Engineering

King Abdulaziz University

Slide 188

Star-Delta Connection

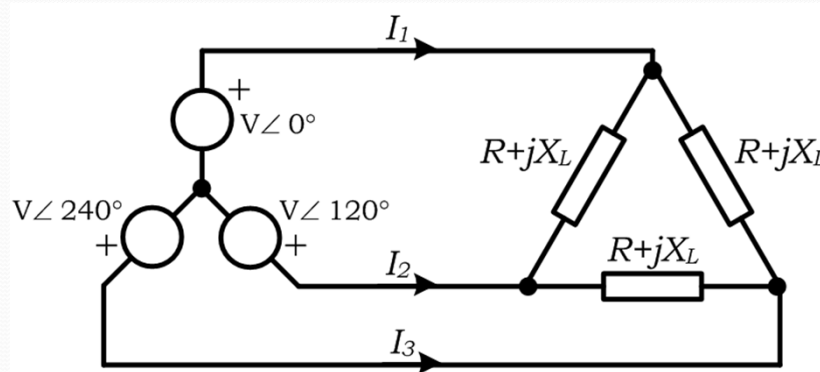

Electrical & Computer Engineering

King Abdulaziz University

Slide 189

Power Factor (PF)



- Best Network when $Q=0$
- Let the angle between Voltage and Current be θ

$$PF = \cos \theta = \begin{cases} 1 & \theta = 0^\circ \\ 0 & \theta = 90^\circ \end{cases}$$

Electrical & Computer Engineering

King Abdulaziz University

Slide 190

Power Factor



- For a single load:

$$Z = R + jX_L$$


- The power factor can be expressed as:

$$PF = \frac{R}{\sqrt{R^2 + X_L^2}}$$

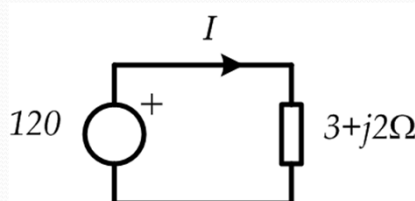Example



- What is the power factor of the circuit shown?




- Solution:

$$PF = \frac{R}{\sqrt{R^2 + X_L^2}} = \frac{3}{\sqrt{3^2 + 2^2}} = 0.832$$

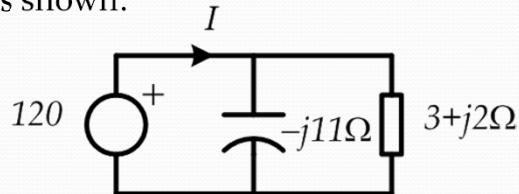Example

- Recalculate the power factor when a capacitor is added as shown:




- Solution:

$$Z_{eq} = (3 + j2) // (-j11) = 4.03 + j1.1$$

$$PF = 0.964$$

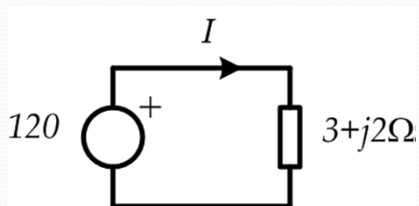
Example

- Calculate the Power and the total Volt-Ampere (S)?



$$I = \frac{120}{3 + j2} = 33.3 \angle -34^\circ$$


$$S = I^* \cdot V = 3310 + j2233$$

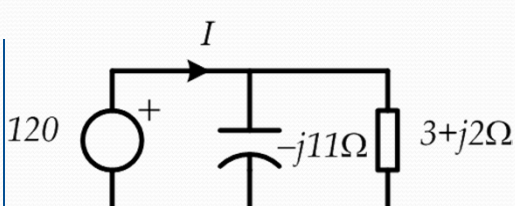

$$I = \frac{120}{4.03 + j1.1} = 28.7 \angle -15^\circ$$

$$S = I^* \cdot V = 3327 + j891$$

Simulation

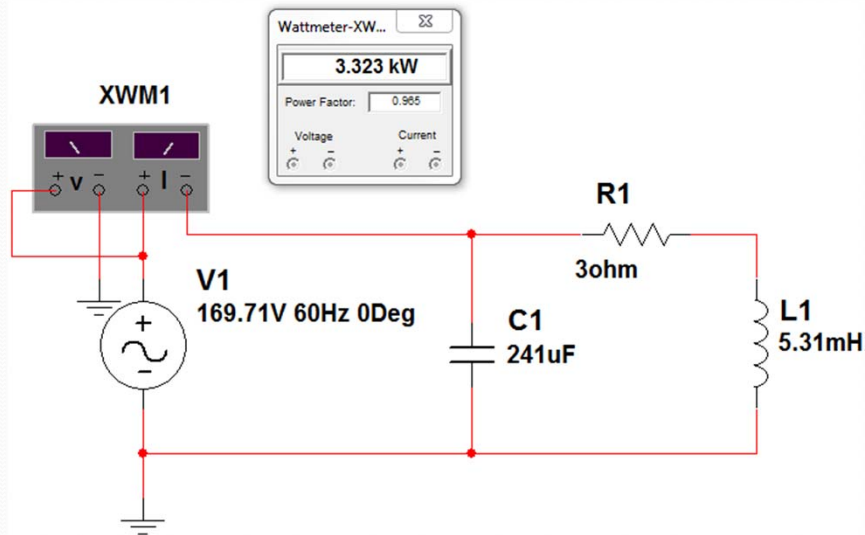

Electrical & Computer Engineering

King Abdulaziz University

Slide 195

Power Factor Correction

- How much parallel Capacitance to improve PF ?

$$X_C = \left(X_L \cdot PF_{new} + R \cdot \sqrt{1 - PF_{new}^2} \right) \times \frac{PF_{new}}{PF_{new}^2 - PF_{old}^2}$$

- Example:

- $Z_L = 3 + j2$
- $PF_{new} = 0.964$


$$X_C = \left(2 \times 0.964 + 3 \times \sqrt{1 - 0.964^2} \right) \times \frac{0.964}{0.964^2 - 0.832^2} = 11$$

Electrical & Computer Engineering

King Abdulaziz University

Slide 196

Star-Start Connection

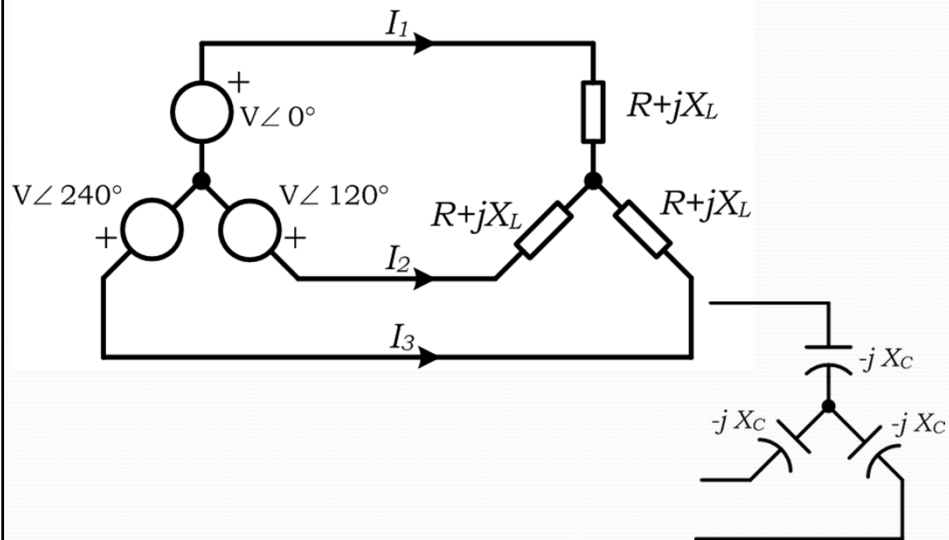


Electrical & Computer Engineering

King Abdulaziz University

Slide 197

Star-Delta Connection

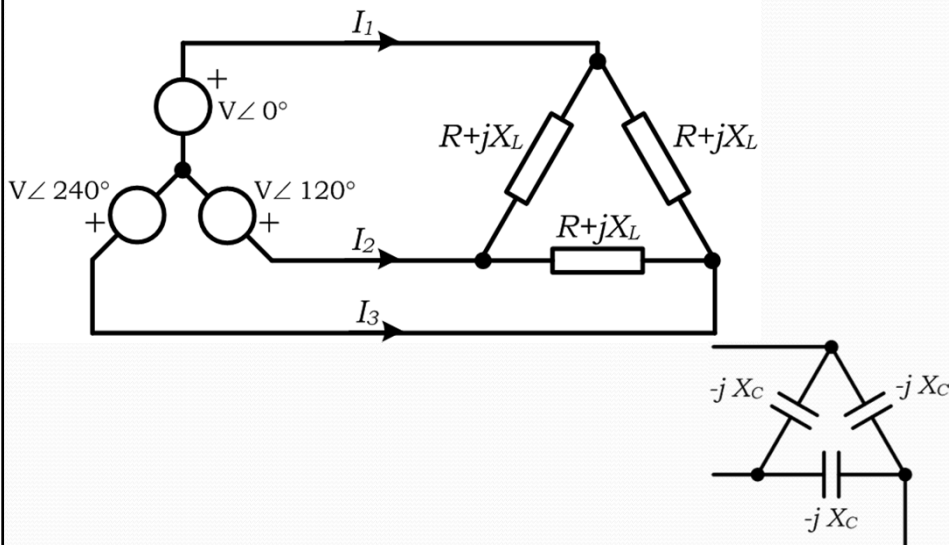

Electrical & Computer Engineering

King Abdulaziz University

Slide 198