

بسم الله الرحمن الرحيم

إخواني الطلاب...

السلام عليكم ورحمة الله وبركاته..

تجدون في هذا المستند حلول المسائل التي وردت في تجارب المعمل و هي:

- 1- Experiment # 3 : Real Power and Reactive Power.
- 2- Experiment # 4 : Power Flow and Voltage Regulation of a Simple Transmission Line.
- 3- Experiment # 5 : Current Transformer (Burden).

و نظرا لقلّة المسائل قمت باختيار أفضل الإجابات التي وردت في تقاريركم و وضعها كحلول لهذه المسائل مع كتابة اسم صاحب الحل و ليس لسبب إلا تقديرا - لهم و للجميع - على مجهوداتكم الرائعة خلال هذا الفصل الدراسي.

الكل يستحق الإشادة و الشكر .. فشكرا لكم..

أخوكم

م. فهد حريري

Solutions

Experiment # 3 : Real Power and Reactive Power

Answer of Q.1: (by: [Eng. Rayan Al-Amoudi](#))

Direction of real and reactive power flow with Ideal element load			
	Load	Real Power	Reactive Power
a	Resistance	+VE	0
b	Inductance	+VE	+VE
c	Capacitance	0	-VE
d	Resistance & Inductance	+VE	+VE
e	Resistance & Capacitance	+VE	-VE

Answer of Q.2: (by : [Eng. Emad Al-Zahrani](#))

a) $S = \frac{V^2}{Z^*}$

$V = 120 \text{ V},$

$Z^* = 40 - j 30 \Omega,$

$$S = \frac{120^2}{40 - j 30} = 230.4 + j 172.8 \text{ VA}$$

P = 230.4 W,

Q = 172.8 var.

b) $S = \frac{V^2}{Z^*}$

$V = 120 \text{ V},$

$$Z = 40 // (j60 // -j90) = 40 // j180 = 38.118 + j 8.47 \Omega$$

$Z^* = 38.118 - j 8.47 \Omega$

$$S = \frac{120^2}{38.118 - j 8.47} = 360 + j 80 \text{ VA}$$

P = 360 W, **Q = 80 var.**

Answer of Q.3: (by : [Eng. Mansoor Al-Zahrani](#))

$$I = \frac{\frac{69k}{\sqrt{3}} \angle 0}{100 \angle 0} = 398.37 \angle 0 \text{ A}$$

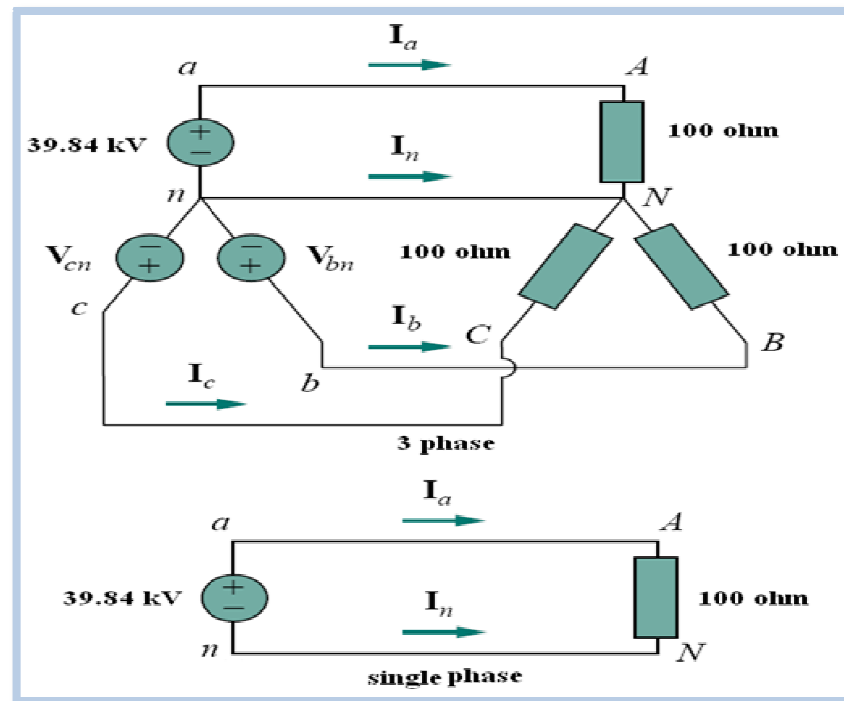


Fig. : Question no. 3 circuit.

$$\text{Complex power}(3\phi) = 3V_{L-N} I^* = 3 \left(\frac{69k}{\sqrt{3}} \angle 0 \right) (398.37 \angle 0) = 47.610 \angle 0 \text{ MVA}$$

$$\text{Complex power}(S_{3\phi}) = 47.610 + j0 = +P + jQ \text{ MVA}$$

$$\underline{P = +47.6 \text{ MW}}$$

Answer of Q.4: (by : [Eng. Fahd Hariri](#))

Power flows into the inductor.

Power flows out of the capacitor.

Answer of Q.5: (by : [Eng. Mohammad Bahadeg](#))

$$\text{Line KW} = \text{KW}_1 - \text{KW}_2$$

$$\text{Line Kvar} = \text{Kvar}_1 - \text{kvar}_2$$

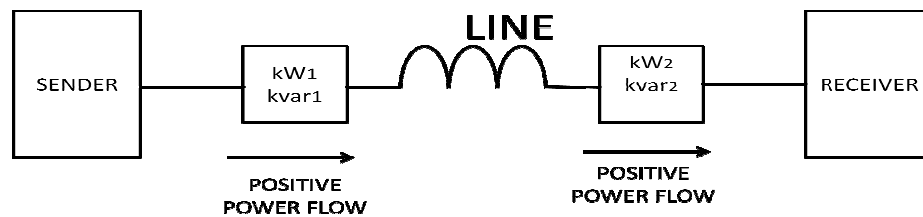


Fig. Transmission line inductor model

kW1	Kvar1	kW2	Kvar2	LINE kW	LINE kvar
+100	+95	+5	+5	+5	+5
+100	+95	-10	-10	+5	+20
+100	+95	-25	-25	+5	+15
-100	-105	+5	+5	+5	+5

Answer of Q.6: (by : [Eng. Sultan Al-Ghamdi](#))

$$P = 3 E_p I_p = 3 * \frac{E}{\sqrt{3}} * \frac{E}{\sqrt{3} * Z} = \frac{E^2}{Z}$$

Experiment # 4 : Power Flow and Voltage Regulation of a Simple Transmission Line

Answer of Q.1: (by : Eng. Badr al-jehani)

a) The line-to-neutral voltage per phase.

$$V_{ph} = \frac{V_L}{\sqrt{3}} = \frac{70000 \text{ V}}{\sqrt{3}} = \mathbf{40410 \text{ V}}$$

b) The line current per phase.

$$I_{Line} = \frac{V_{ph}}{z} = \frac{40410 \text{ V}}{160 + j120} = \mathbf{202.05 \text{ A}}$$

c) The real and reactive power supplied to the load.

$$P_{Load(3\phi)} = 3P_{Load(1\phi)} = \mathbf{19595.6 \text{ kW}}$$

$$Q_{Load(3\phi)} = 3Q_{Load(1\phi)} = \mathbf{0 \text{ VAR}}$$

d) The real and reactive power absorbed by the line.

$$P_{Line(3\phi)} = 3P_{Line(1\phi)} = \mathbf{0 \text{ W}}$$

$$Q_{Line(3\phi)} = 3Q_{Line(1\phi)} = \mathbf{14696.7 \text{ kVAR}}$$

e) The line-to-line voltage at the load.

$$V_{Load(line)} = \sqrt{3} V_{load(ph)} = 55993.7 \text{ V} = \mathbf{56 \text{ KV}}$$

f) The voltage drop per phase in the line.

$$V_{LD} = I_{Line} * Z_{line} = 202.05 \angle (-0.644 \text{ rad})(j120) = 24246 \text{ V} = \mathbf{24.2 \text{ KV}}$$

g) The total apparent power supplied by the source.

$$S_{(ph)} = I_{rms} V_{rms} = 202.05 (40410 \text{ V}) = 8164 \text{ kVA}$$

$$S_{(3ph)} = 3S_{(ph)} = 3(8164) = \mathbf{24494 \text{ kVA}}$$

h) The total real and reactive power supplied by the source.

$$S_{(ph)} = \sum P + j \sum Q$$

$$= (6531.9 \text{ kW}) + j(4898.9 \text{ kVAR}) = 8164 \angle (0.64 \text{ rad}) \text{ kVA}$$

$$S_{(3ph)} = 3S_{(ph)} = 3(8164 \angle (0.64 \text{ rad})) = \mathbf{19595.7 + j14696.7 \text{ kVA}}$$

Answer of Q.2: (by [Eng. Rayan Al-Amoudi](#))

A)

Since R is open the we neglect j120 therefore the voltage across R is the same as the voltage across C

$$V_R = V_C = \frac{-j600}{-j600 + j120} \times 330kv = 412.5kv$$

B)

$$S = 3 * V * I^* = 3 * \frac{330k}{\sqrt{3}} * \left(\frac{\frac{330k}{\sqrt{3}}}{j120 - j600} \right)^* = -226.874645j VA$$

$$Q = -226.874645 Mvar$$

Or

$$Q = 3 * |I|^2 * X = 3 * 396.928^2 * (j120 - j600) = -226.875 Mvar$$

And since the power is -ve (the power absorbed by the source)

Experiment # 5 : Current Transformer (Burden)

Answer of Q.2: (by [Eng. AbdulRaheem AL-Obaidi](#))

Total burden = cable burden+ burden of relay

Case 1

Rated burden of relay = 0.1 VA

$$\text{Cable burden} = \frac{2 \cdot l \cdot c \cdot p \cdot I_{sc}^2}{A} = \frac{2 \cdot 50 \cdot 0.0203104 \cdot 1}{4} = 0.50776 \text{ VA}$$

$$\text{Total burden} = 0.50776 \text{ VA} + 0.1 \text{ VA}$$

$$= 0.606776 \text{ VA}$$

In case 2 the burden is equal burden in case 1 because the I_s in case 1 equal I_s in case 2.

Since $P_{\text{total}} < P_n$

Therefore the C.T can handle the burden of the relay and the cables.