
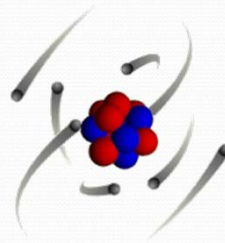


Basic Concepts


Section 02

Electrons

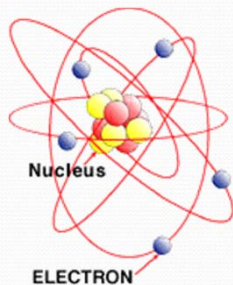- Atoms and Electrons
- Heat and Free Electrons



Is It Like This?!

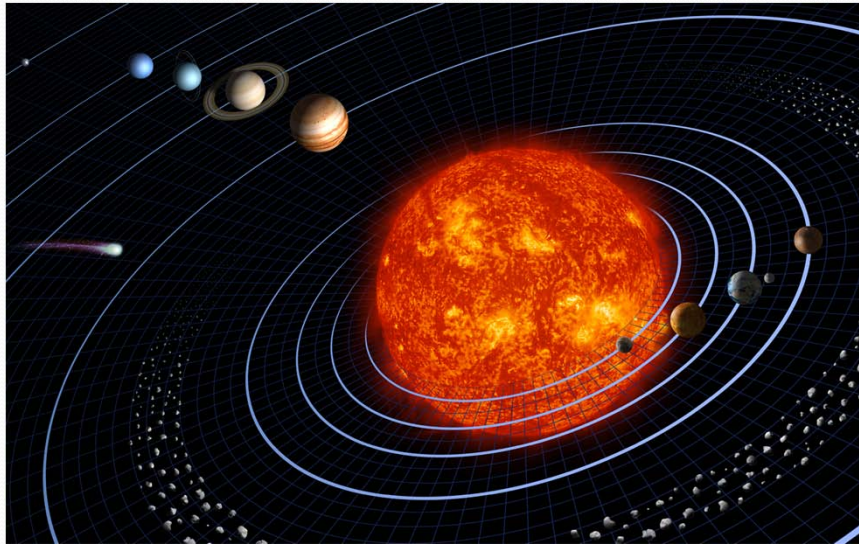

Electrical & Computer Engineering


King Abdulaziz University

Slide 33

Electricity



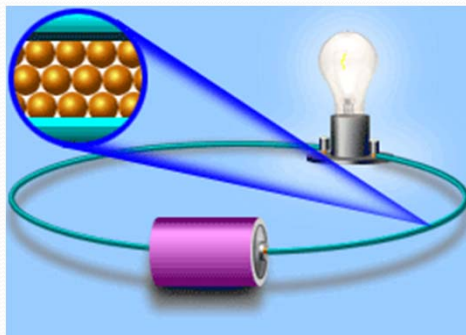- If electrons were pushed, they produce a current



Electrical & Computer Engineering

King Abdulaziz University

Slide 34

Battery



- Source of pushing electrons
- Electrochemical reactions
- Look for types of batteries in Wikipedia!!



Volt



- Alexander Volta (first battery)
- Electromotive Force
 - 1.5V, 110V, 13.8kV






Model AMA-100



AC and DC Currents



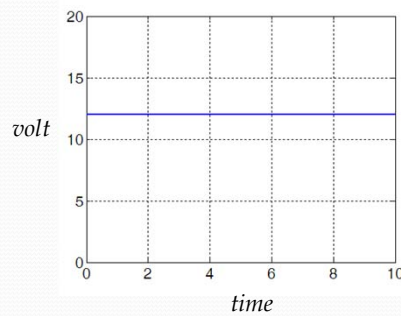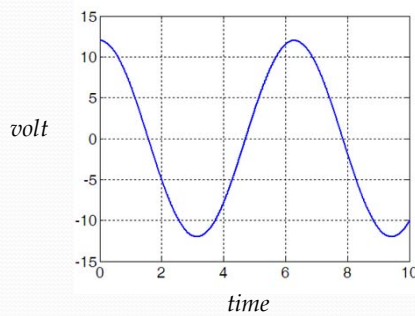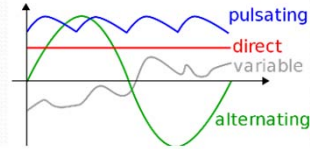- Cascade 73 batteries in series. Do they generate 110V?
 - DC: direct current
 - AC: alternating current



Electrical & Computer Engineering

King Abdulaziz University




Slide 37

Frequency of AC Signal



- Frequency = Number of cycles per second

$$f = \frac{1}{T}$$

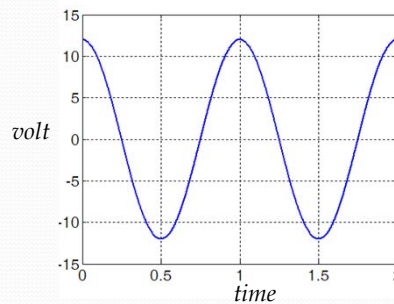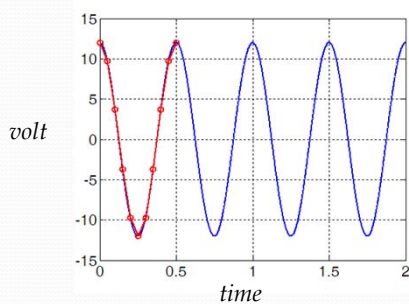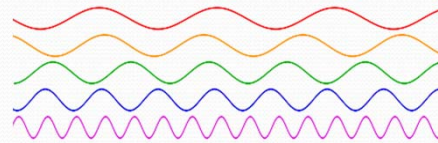

Electrical & Computer Engineering

King Abdulaziz University

Slide 38




Experiment!!

- What's the highest frequency your eyes can notice?
 - *frequency vs. amplitude..*
- What is the frequency of 110V battery?




Closed Loop Circuits

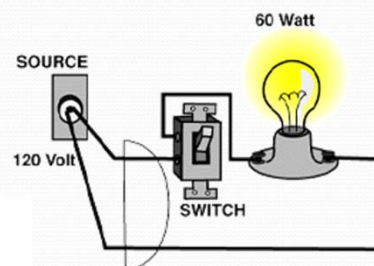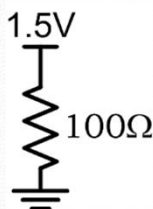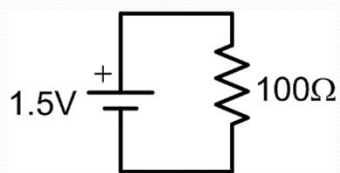- No current will flow in an open loop circuit..



Closed Loop Circuits

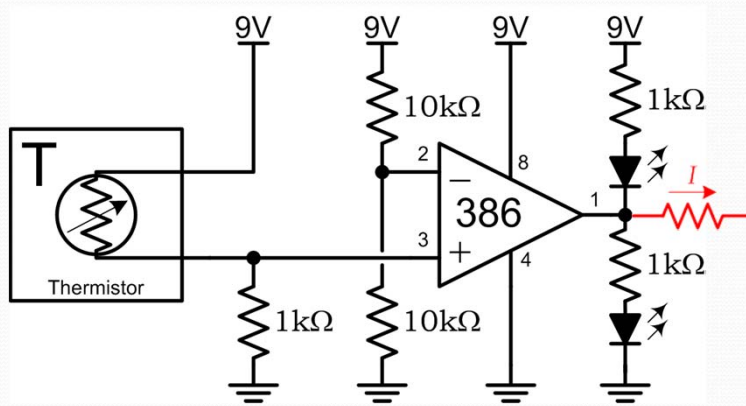


Electrical & Computer Engineering

King Abdulaziz University

Slide 41

Ground Currents

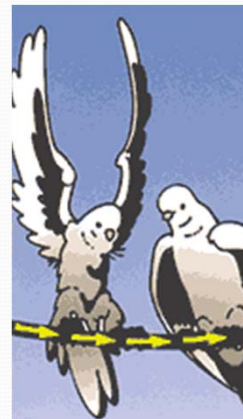1. Why birds do not get shocked by high voltage lines?
2. Can you safely touch one node of home electricity?
3. What about lightening?



Electrical & Computer Engineering

King Abdulaziz University

Slide 42

Current





- Number of electrons passing every second
- Ampere (A) is a unit of current
 - 1 A = 6.28×10^{18} electrons/sec
- At home: 60A, 100A (20A per phase)
- Electronics: 10mA

AC Source



- Generally produces sine wave

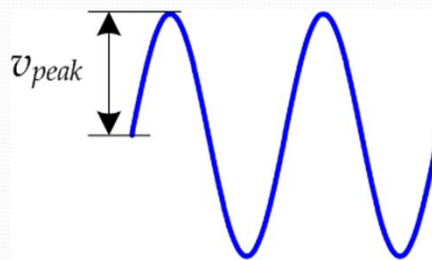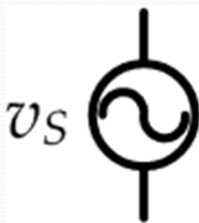

$$v_s = v_{peak} \times \sin(\omega \times t)$$

$$v_s = v_{peak} \times \sin(2\pi \times f \times t)$$

RMS



- RMS: Root Mean Square
 - power is measured instead of peak voltage

$$V_{RMS} \equiv \sqrt{\frac{1}{T} \int_0^T v^2(t) \cdot dt}$$

- for sine or cosine signals, $v(t) = A \cos(2\pi t/T)$

$$V_{RMS} = \frac{v_{peak}}{\sqrt{2}}$$



RMS



- If your meter reads $10V_{\sim}$
 - then $v_{peak} = 10 * 1.4 = 14V$
- If your peak voltage is $154V_p$
 - then the meter reads $RMS = 154 * 0.7 = 110V_{\sim}$